
EE288 Data Conversions/Analog Mixed-Signal ICs

Spring 2020

Project Description

May 11, 2020


Prof. Sang-Soo Lee
sang-soo.lee@sjsu.edu
ENG-259

Target Spec

You may not be able to meet all the target spec.
Do your best to meet the spec as much as you can.

▪ Process Technology	45nm CMOS with 1V device only
▪ Supply Voltage	VDD = 1V
▪ Resolution	8 bits
▪ Sampling Rate, fs	10 MS/s
▪ Input Range, VFS	1.2 Vppd
▪ Input Frequency	$(7/64) \cdot f_s$ MHz
▪ Input Clock, MCLK	100 MHz with 0.1ns rise and fall time
▪ Walden FoM	10 fJ/conversion-step

Differential Input Signal

 

Project Logistic

- Due May 16, 11PM
- 2 students per group
- Single student per group is fine
- Reference schematics: **Async_SAR_ADC_tb2 in 288lib**
- Score - 25% of the total course score
 - Report in IEEE format & neatness 20%
 - Verilog-A code for every block 20%
 - Clear Transistor level schematics 20%
 - Functionality and performance 20%
 - **Design1CIDxxyy.tbz2 file will be used to check the circuit function**
 - Additional effort and creativity 20%

Project Submission

Report file - **EE288ReportCIDxxyy.pdf**

- Prepare your project report in IEEE 2-column Word format
- Total pages should be between 4 and 6 pages
- Include the following sections in the report
Abstract, Introduction, Circuit Design, Simulation Results, Conclusions, References

Slide file - **EE288SlideCIDxxyy.pdf**

- Include as many additional pages as you like in power point slide format
- Include Verilog-A codes, schematics, simulation setup and results

Design file - **Design1CIDxxyy.tbz2**

- Create Design1.tbz2 and rename it to Design1CIDxxyy.tbz2
- See the instruction described in EE288_Design_file_for_Instructor_Review.pdf

Submission

- **Upload 3 files to Canvas** by 11PM on the due date
- File name:
 - **EE288ReportCIDxxyy.pdf**
 - **EE288SlideCIDxxyy.pdf**
 - **Design1CIDxxyy.tbz2**

where xx and yy are CIDs of your group

Implementation Detail

■ Architecture

- Fully-differential Asynchronous SAR
- Top-plate sampling with monotonic switching scheme
- Use VDD as VREF
- Assume 100MHz Ideal clock with reasonable clock edges

■ Capacitive DAC

- Optimize the unit capacitor value based on kT/C noise, mismatch, and other considerations
- Optimize the top plate parasitic capacitor value, CH
- Choose switches based on RC delay, linearity, and switching scheme to optimize power

■ Comparator

- Design comparator based on the offset you can tolerate for the SAR ADC
- You must simulate the comparator separately to ensure functionality

■ Asynchronous clock generator

- You should optimize the delay timing between Clkc and Valid
- You can try a different asynchronous circuit to optimize the overall design

■ SAR Logic

- You should implement the SAR logic in Verilog code first and then in transistor level

Simulations


- Run at the following simulation condition
 - Process TT
 - Voltage 1 V
 - Temperature 27 C
- Use an ideal DAC to create FFT spectrum of the ADC with an input frequency of $(7/64) \cdot f_s$ MHz
- Report dynamic and static performance as well as ADC figure of merit based on $\text{FoM} = \text{Power} / (f_s \times 2^{\text{EBOB}})$

References


1. Olga Kardonik, *MS Thesis, University of Texas, Austin*, A study of SAR ADC and implementation of 10-bit asynchronous design, 2013
2. Albert Hsu Ting Chang, *PhD Thesis, MIT*, Low-power high-performance SAR ADC with redundancy and digital background calibration, 2013
3. C. Liu, S. Chang, G. Huang, Y. Lin, “A 10-bit 50-MS/s SAR ADC with a monotonic capacitor switching procedure,” *IEEE J. Solid-State Circuits*, pp. 731–740, April 2010
4. Pieter Harpe, Cui Zhou, et. al. “A 26 W 8 bit 10 MS/s asynchronous SAR ADC for low energy radios,” *IEEE J. Solid-State Circuits*, pp. 1585–1595, July 2011
5. T. Cao, S. Aunet, T. Ytterdal, “A 9-bit 50MS/s asynchronous SAR ADC in 28nm CMOS,” [NORCHIP 2012](#)
6. Brian P. Ginsburg and Anantha P. Chandrakasan, “An energy-efficient charge recycling approach for a SAR converter with capacitive DAC,” *IEEE ISCAS* 2005
7. Victor Gylling, *MS Thesis, Lund University, Sweden*, Implementation of a 200 MSps 12-bit SAR ADC, 2015

10-bit SAR ADC Example

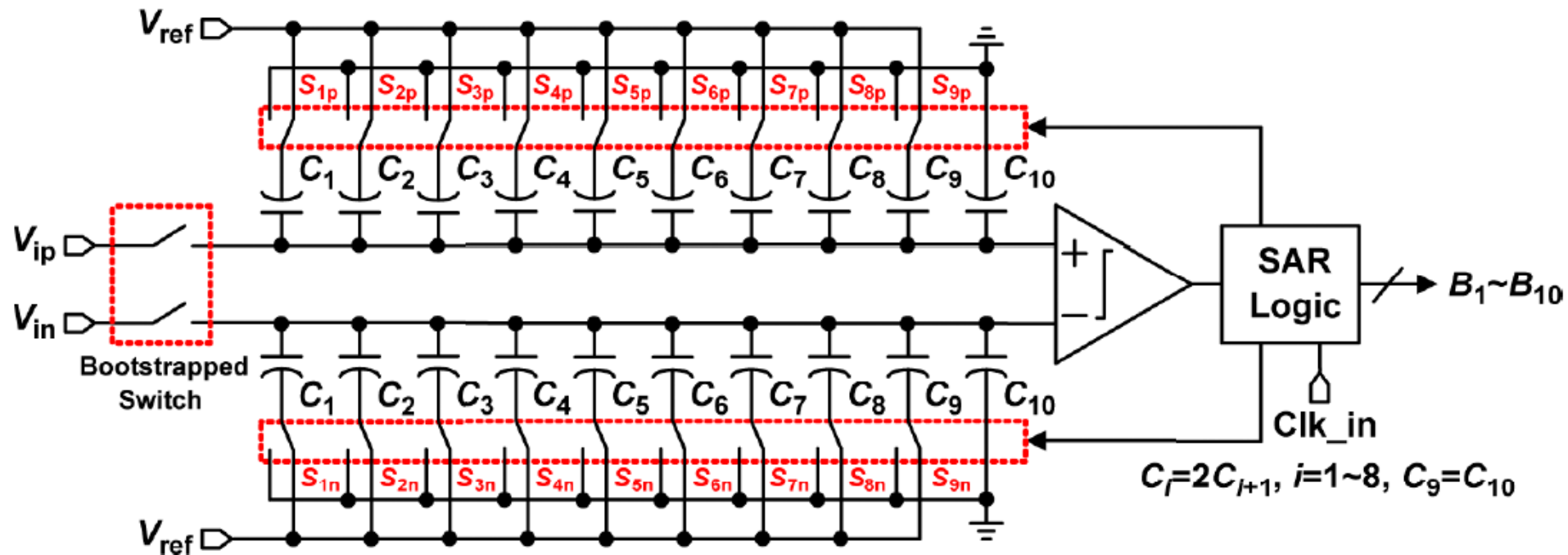
C. Liu, S. Chang, G. Huang, Y. Lin, "A 10-bit 50-MS/s SAR ADC with a monotonic capacitor switching procedure," *IEEE J. Solid-State Circuits*, pp. 731–740, April 2010



Async_SAR_ADC_tb2 in 288lib

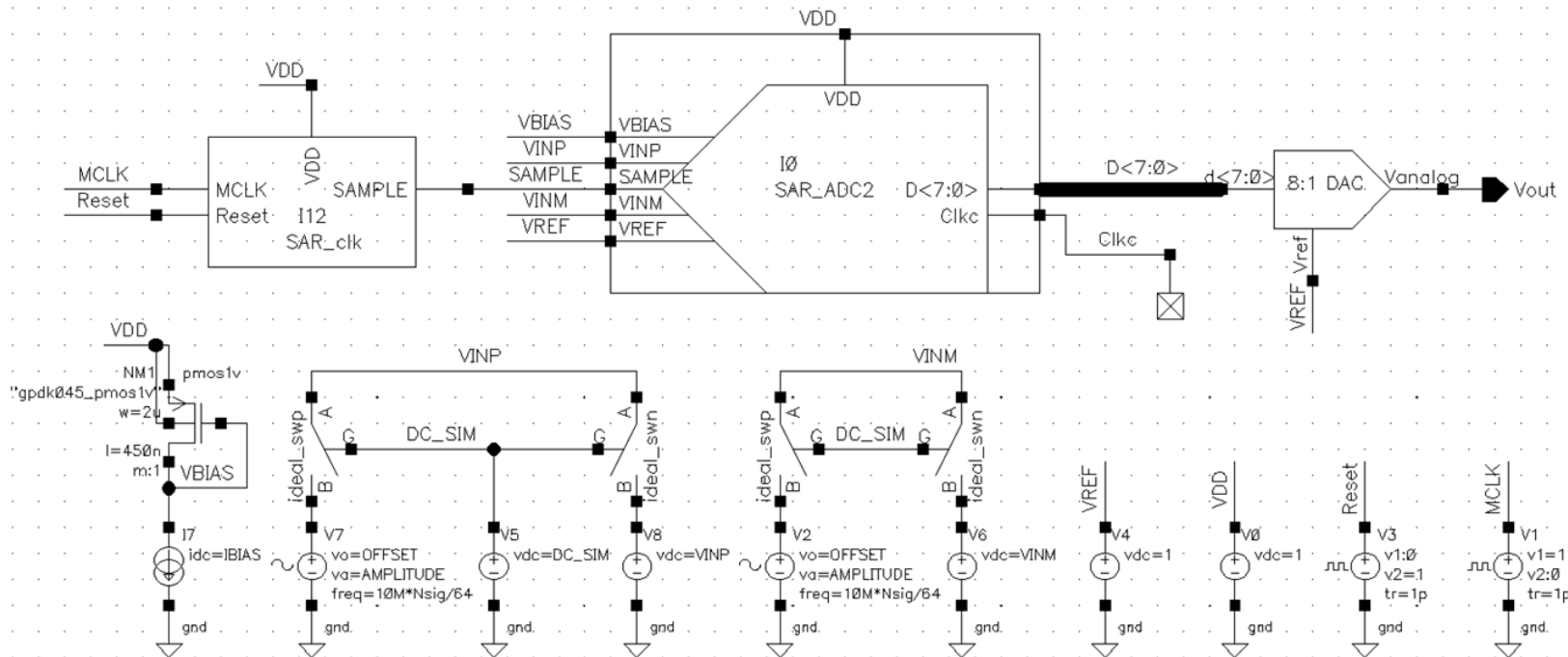


SAR_ADC2

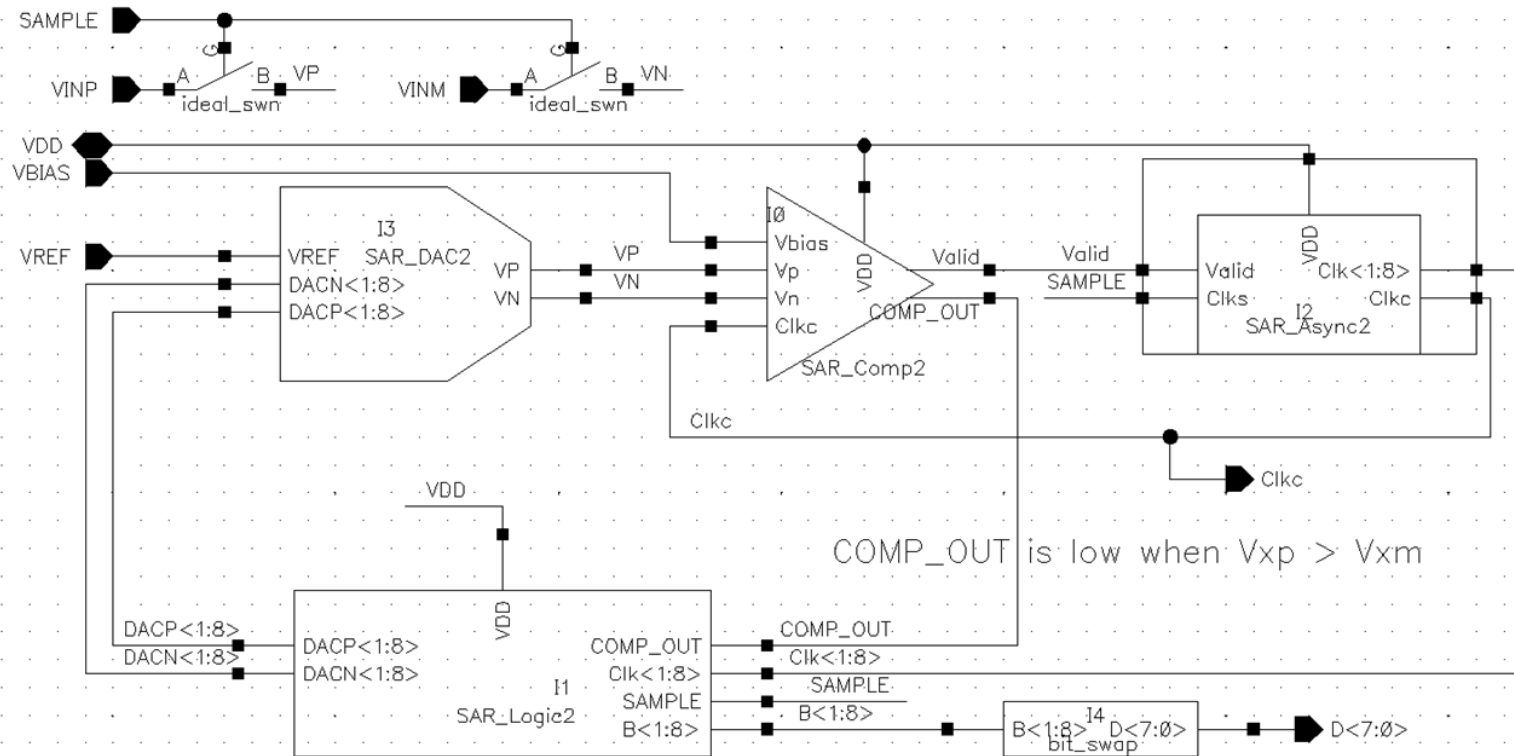

Monotonic Switching Scheme



B<1>=MSB..... B<8>=LSB

8-bit DAC Array with C_H

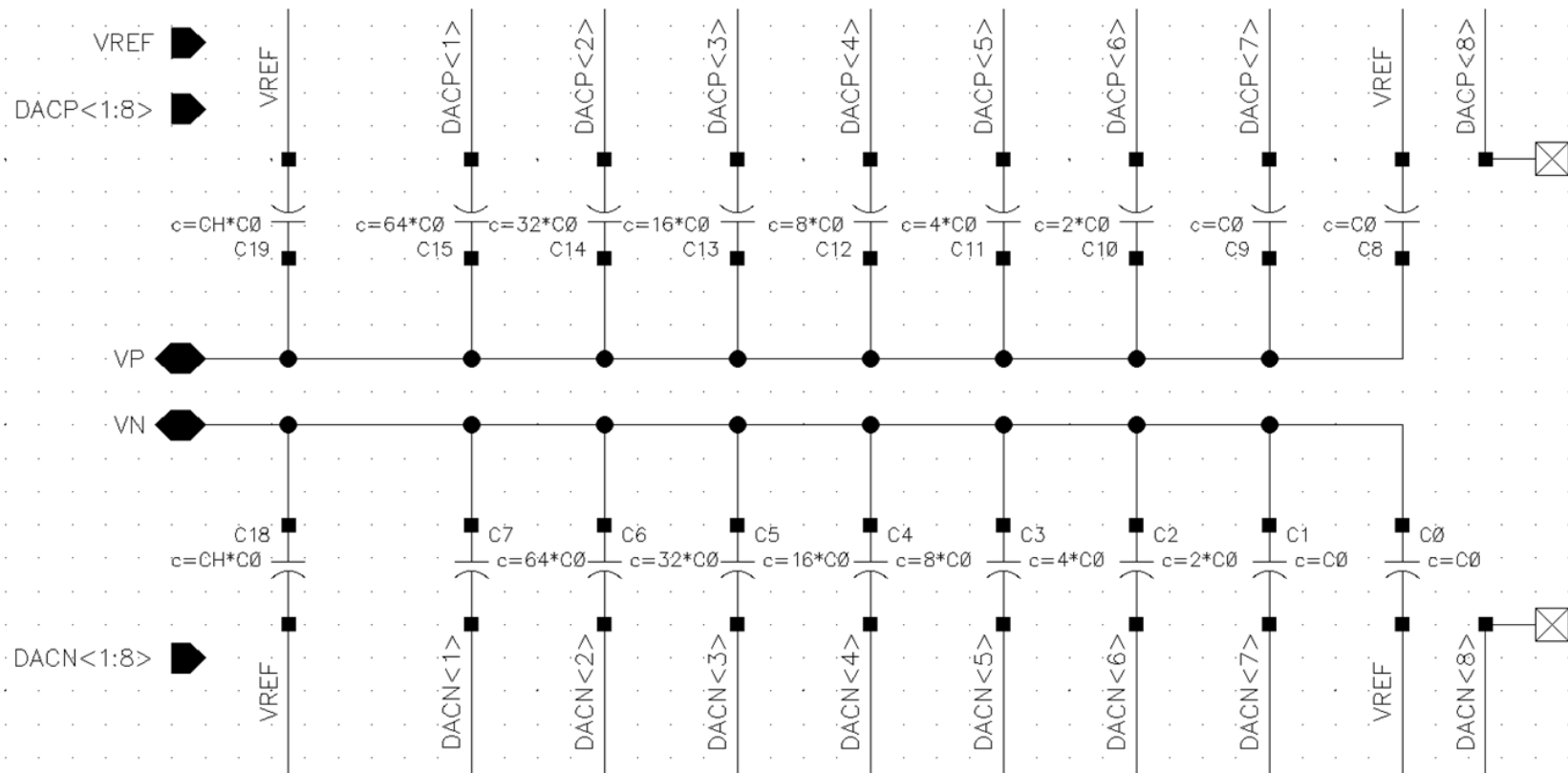

Bootstrapped Switch Example

 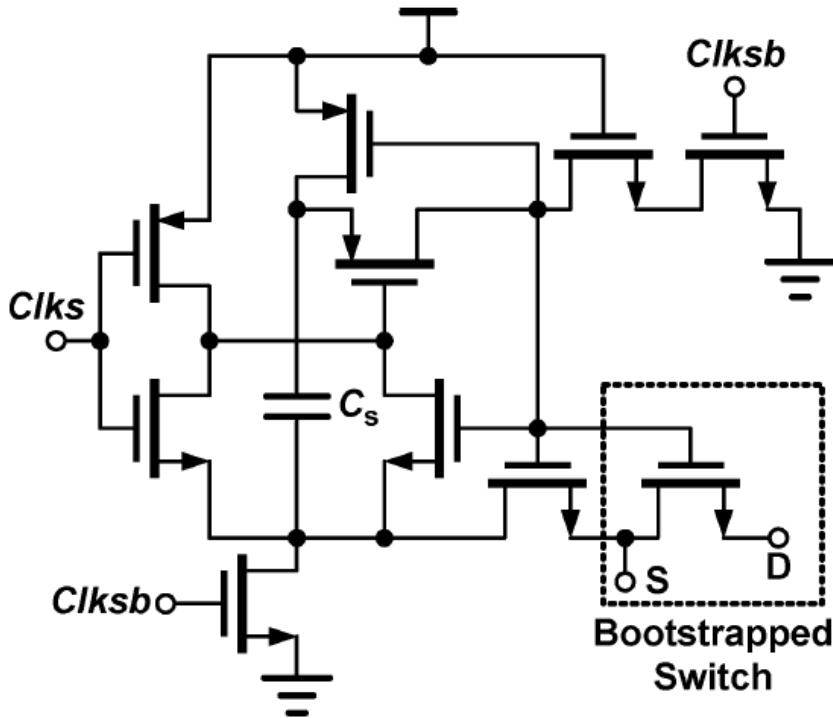
C. Liu, S. Chang, G. Huang, Y. Lin, "A 10-bit 50-MS/s SAR ADC with a monotonic capacitor switching procedure," *IEEE J. Solid-State Circuits*, pp. 731–740, April 2010






**Will not be required to use bootstrapped switch in the project
→ Use ideal_swn**

Dynamic Comparator Example

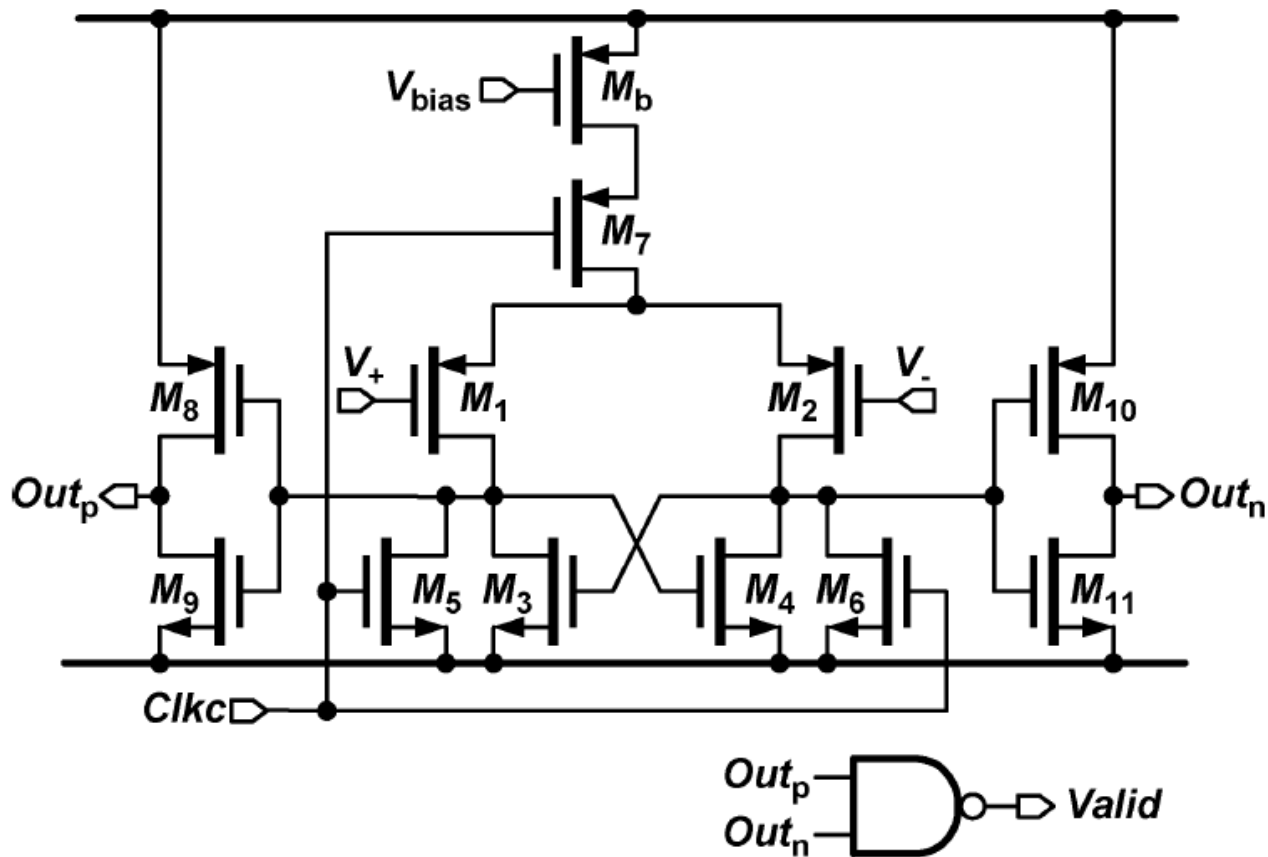
C. Liu, S. Chang, G. Huang, Y. Lin, "A 10-bit 50-MS/s SAR ADC with a monotonic capacitor switching procedure," *IEEE J. Solid-State Circuits*, pp. 731–740, April 2010




Flow Chart and Switching Schemes

  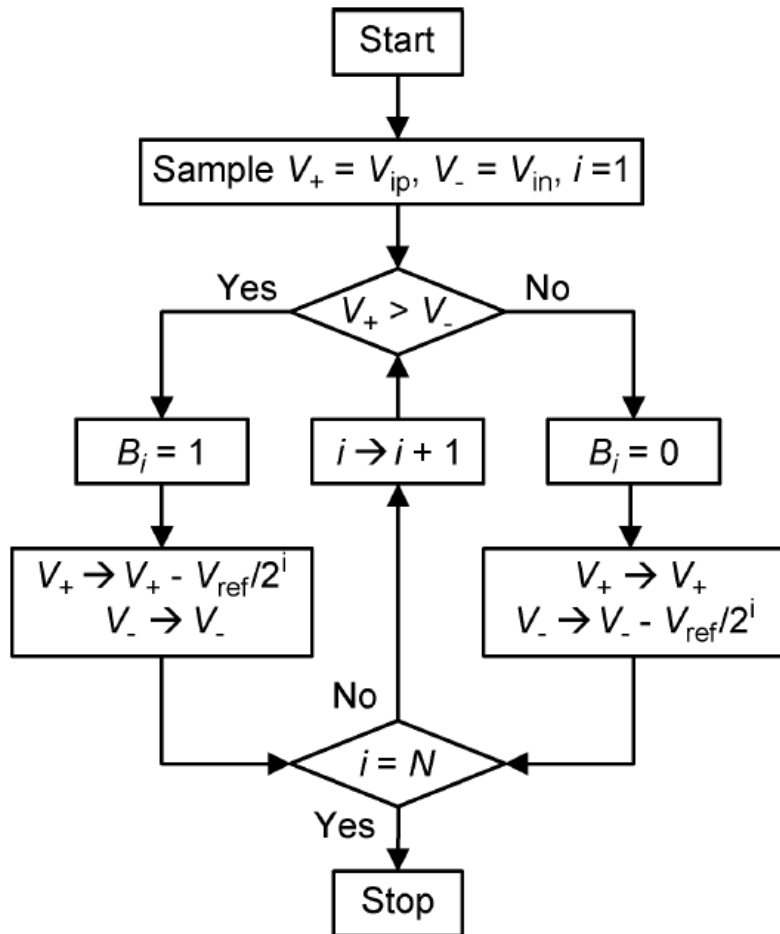

Conventional Switching Scheme

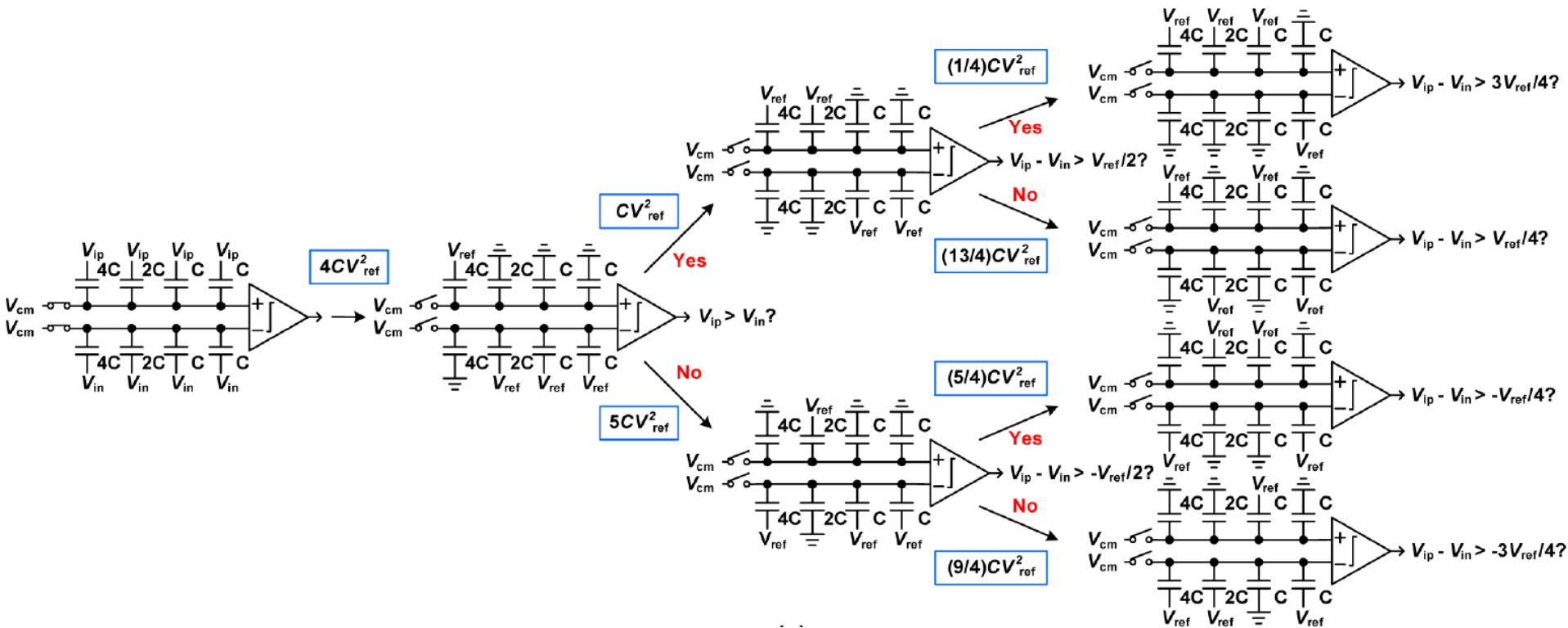


Monotonic Switching Scheme

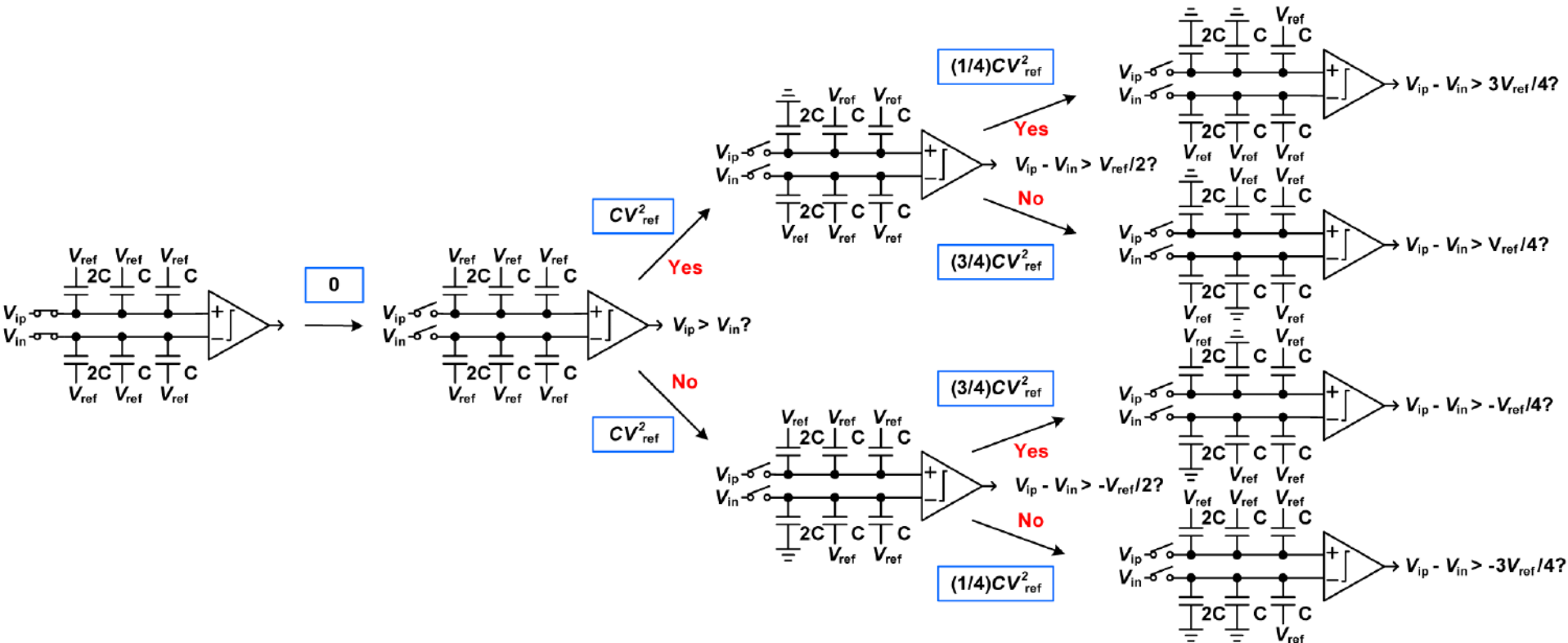

Switching Energy vs Output Code

 C. Liu, S. Chang, G. Huang, Y. Lin, "A 10-bit 50-MS/s SAR ADC with a monotonic capacitor switching procedure," *IEEE J. Solid-State Circuits*, pp. 731–740, April 2010




Comparison of Switching Procedures

C. Liu, S. Chang, G. Huang, Y. Lin, "A 10-bit 50-MS/s SAR ADC with a monotonic capacitor switching procedure," *IEEE J. Solid-State Circuits*, pp. 731–740, April 2010

Switching Procedure	Conventional	Split Capacitor	Energy-saving	Proposed
Normalized Switching Power	1	0.63	0.44	0.19
No. of Switches	$4N+10$	$8N+6$	$8N+2$	$4N$
No. of Capacitors	$2N+2$	$4N$	$4N-2$	$2N$
No. of Unit Capacitors in Capacitor Array	2^N	2^N	2^N	2^{N-1}


Asynchronous Control Logic and Timing

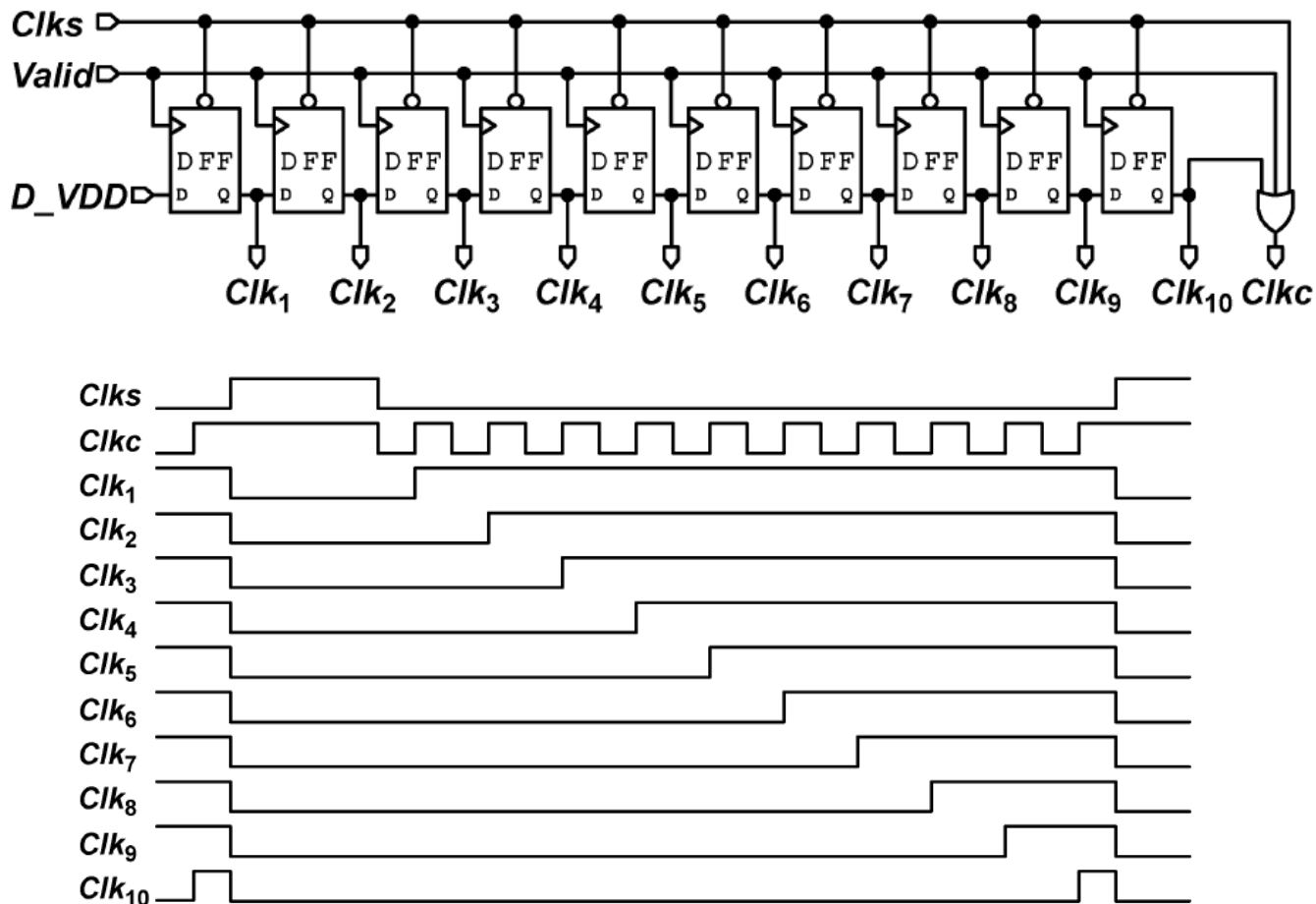C. Liu, S. Chang, G. Huang, Y. Lin, "A 10-bit 50-MS/s SAR ADC with a monotonic capacitor switching procedure," *IEEE J. Solid-State Circuits*, pp. 731–740, April 2010




DAC Control Logic

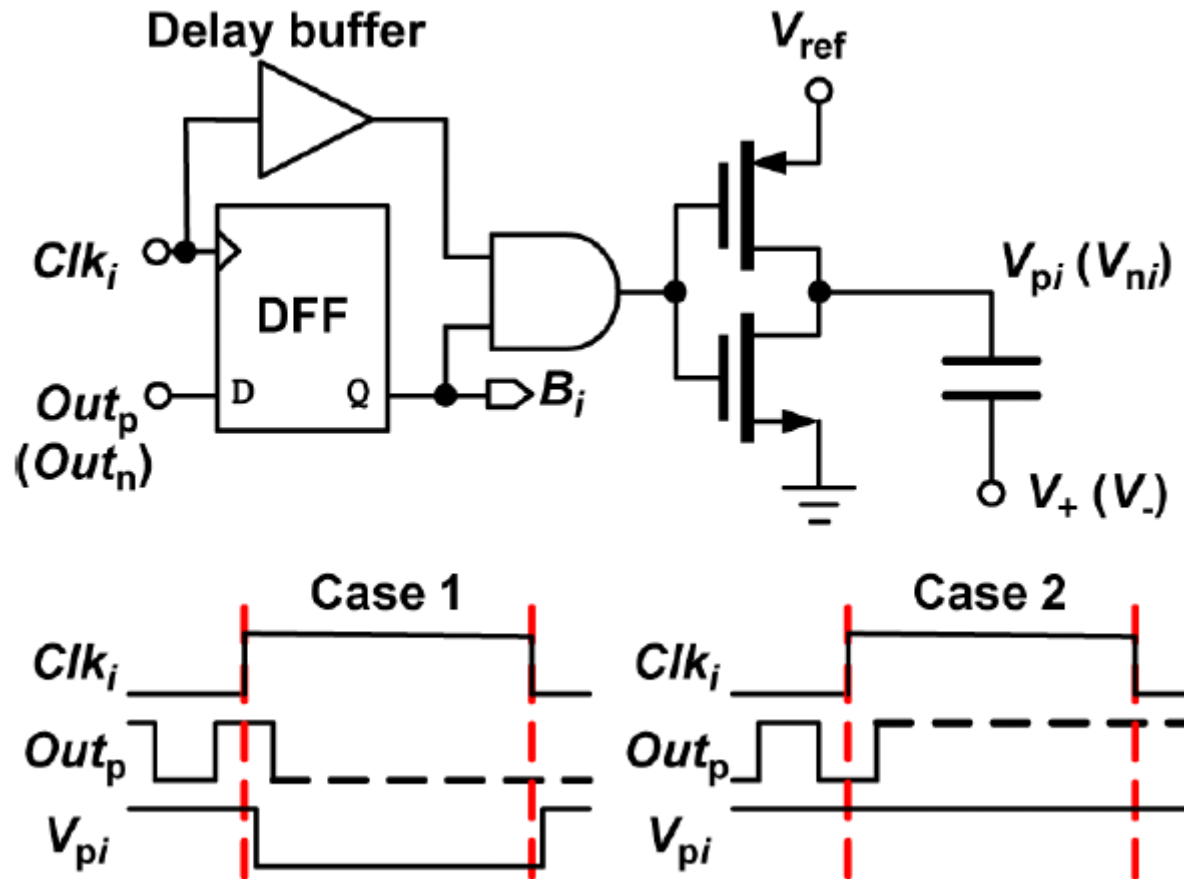C. Liu, S. Chang, G. Huang, Y. Lin, "A 10-bit 50-MS/s SAR ADC with a monotonic capacitor switching procedure," *IEEE J. Solid-State Circuits*, pp. 731–740, April 2010






Change in Asynchronous Control Logic and Timing

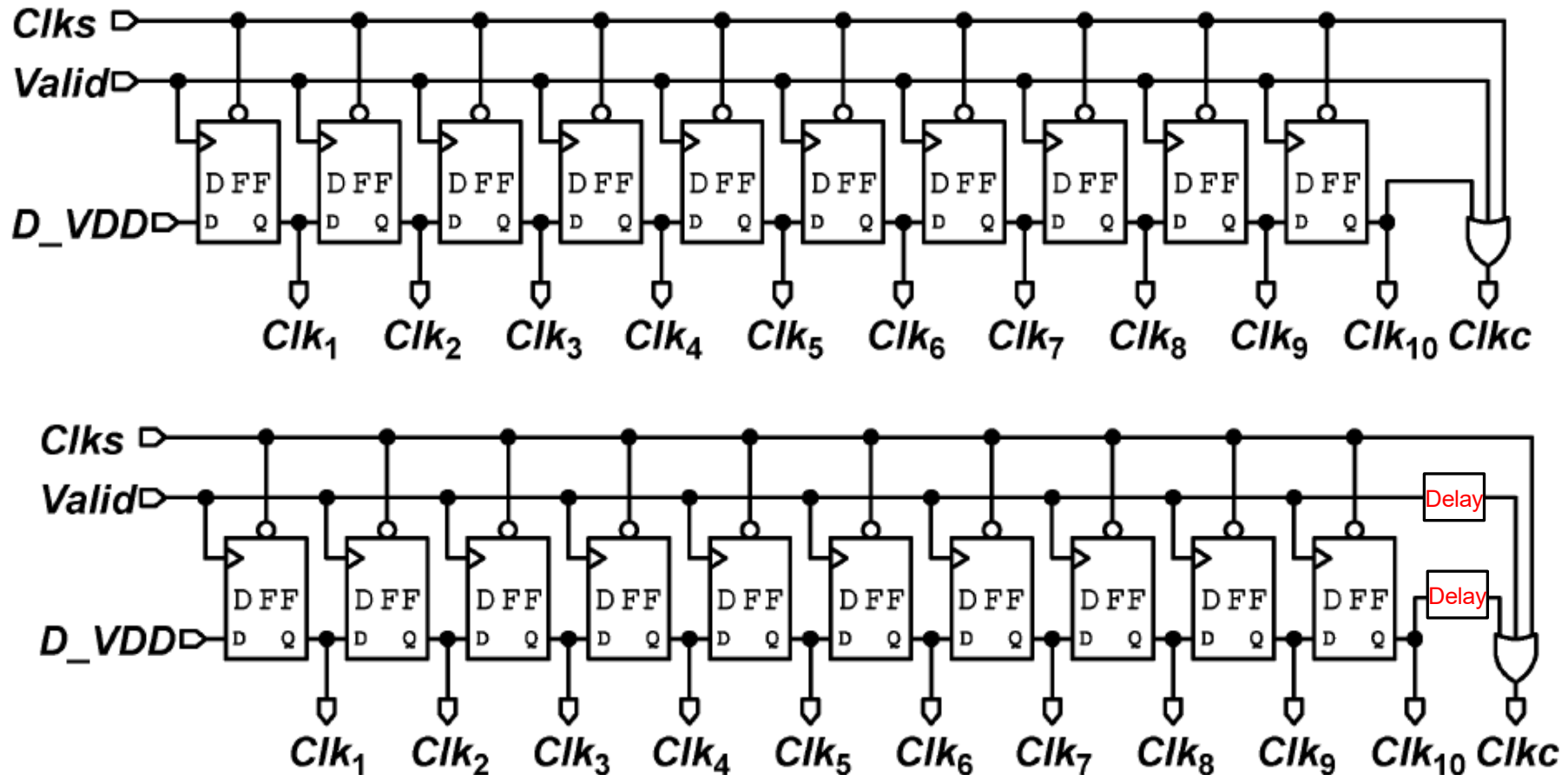C. Liu, S. Chang, G. Huang, Y. Lin, "A 10-bit 50-MS/s SAR ADC with a monotonic capacitor switching procedure," *IEEE J. Solid-State Circuits*, pp. 731–740, April 2010



Change in DAC Control Logic

   

Make sure that **Outp** is settled to a new value before **Clkid** goes high.

ADC Summary

C. Liu, S. Chang, G. Huang, Y. Lin, “A 10-bit 50-MS/s SAR ADC with a monotonic capacitor switching procedure,” *IEEE J. Solid-State Circuits*, pp. 731–740, April 2010

Specification (Unit)	Experimental Result
Supply Voltage (V)	1.2
Input CM Voltage (V)	0.6
Input Range (V_{p-p})	2
Sampling Capacitance (pF)	2.5
Sampling Rate (MS/s)	50
Active Area (mm ²)	0.052
DNL (LSB)	0.91 / -0.63
INL (LSB)	1.27 / -1.36
SNDR/SFDR (dB)	57.0 / 65.9 (0.5 MHz)
	56.5 / 64.6 (10 MHz)
	54.4 / 61.8 (50 MHz)
ENOB (bit)	9.18
ERBW (MHz)	50
Power (mW)	0.826

 


Fig. 15. Measured ~~32,768~~-point FFT spectrum at 50 MS/s.
64

 


Fig. 16. Measured dynamic performance versus input frequency at 1.2 V and 50 MS/s.

VDD=1V

 


Fig. 17. Measured dynamic performance versus sampling frequency.

Simulation Setup with $C_H = 0$

ADE L (1) - ee288Spring2020 Async_SAR_ADC_tb2 schematic

Launch Session Setup Analyses Variables Outputs Simulation Results Tools Help cadence

27

Design Variables

	Name	Value
1	CH	0
2	Nsig	7
3	DC_SIM	1
4	AMPLITUDE	300m
5	OFFSET	500m
6	TD_Clk8	1n
7	TD_Valid_C...	1n
8	VINP	800m
9	VINM	200m
10	IBIAS	10u
11	C0	10f
12	Ron	1


Analyses

Type	Enable	Arguments
1 tran	<input checked="" type="checkbox"/>	0 150n

Outputs

Name/Signal/Expr	Value	Plot	Save	Save Options
1 Vout		<input type="checkbox"/>	<input type="checkbox"/>	allv
2 VINP		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
3 VINM		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
4 SAMPLE		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
5 I0/VP		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
6 I0/VN		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
7 I0/Valid		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
8 I0/12/Valid_delay		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
9 Clkc		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
10 I0/COMP_OUT		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
11 I0/Clk<1>		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
12 I0/Clk<2>		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
13 I0/Clk<3>		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv

Simulation Result with $C_H = 0$

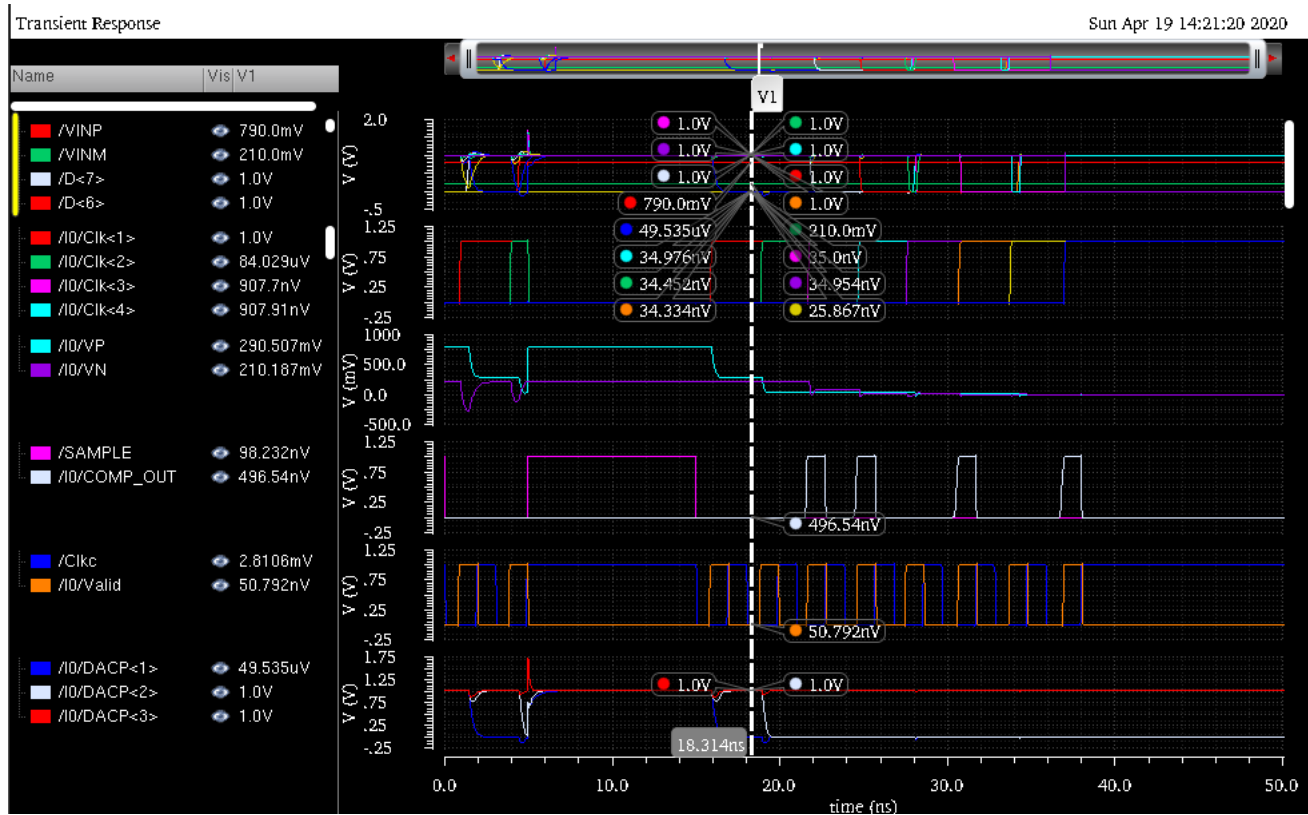

Simulation Setup with $C_H = 85$

ADE L (1) - ee288Spring2020 Async_SAR_ADC_tb2 schematic

Launch Session Setup Analyses Variables Outputs Simulation Results Tools Help cadence

27

Design Variables

	Name	Value
1	CH	85
2	Nsig	7
3	DC_SIM	1
4	AMPLITUDE	300m
5	OFFSET	500m
6	TD_Clk8	1n
7	TD_Valid_C...	1n
8	VINP	790m
9	VINM	210m
10	IBIAS	10u
11	C0	10f
12	Ron	1

Analyses

Type	Enable	Arguments
1 tran	<input checked="" type="checkbox"/>	0 50n

Outputs

	Name/Signal/Expr	Value	Plot	Save	Save Options
1	Vout		<input type="checkbox"/>	<input type="checkbox"/>	allv
2	VINP		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
3	VINM		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
4	SAMPLE		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
5	I0/VP		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
6	I0/VN		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
7	I0/Valid		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
8	I0/I2/Valid_delay		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
9	Clkc		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
10	I0/COMP_OUT		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
11	I0/Clk<1>		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
12	I0/Clk<2>		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
13	I0/Clk<3>		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
14	I0/Clk<4>		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
15	I0/Clk<5>		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
16	I0/Clk<6>		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
17	I0/Clk<7>		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
18	I0/Clk<8>		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
19	D<7>		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv
20	D<6>		<input checked="" type="checkbox"/>	<input type="checkbox"/>	allv

Simulation Result with $C_H = 85$

